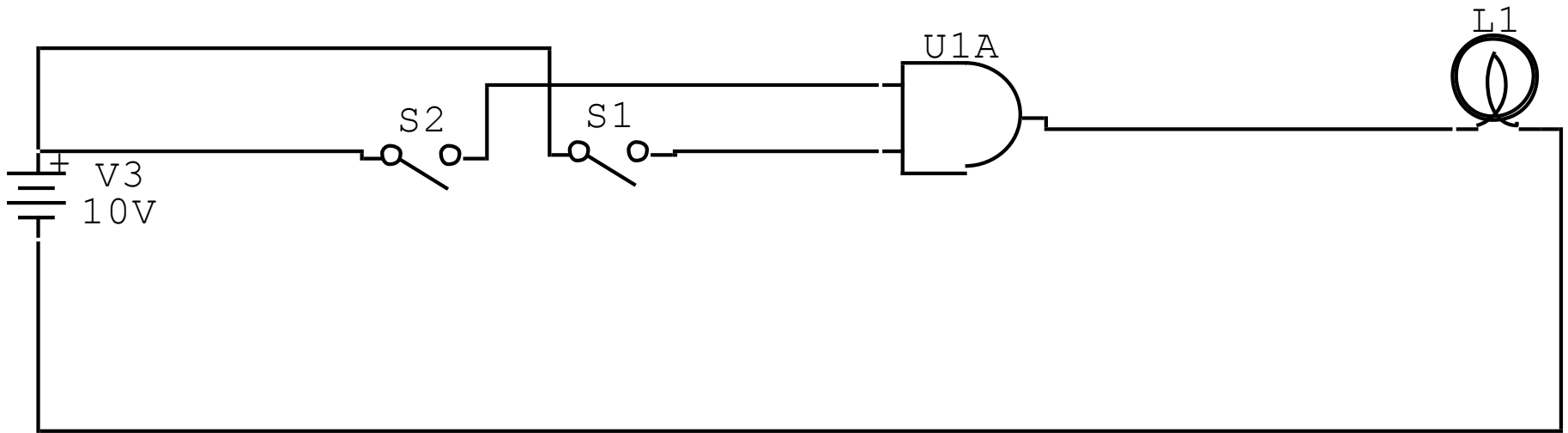



2In AND






Browse Search Digital



Hotkey... Place

- Lamp
- Logic Display
- StopLight
- Motors
- Optical
 - Opto Isolator
- Digital Basics
 - Buffers/Inverters
 - Flip-Flops
 - Gates
 - 2-In AND
 - 2-In NAND
 - 2-In NOR
 - 2-In OR
 - 2-In XNOR
 - 2-In XOR
 - 3-In AND
 - 3-In NAND
 - 3-In NOR
 - 3-In OR
 - 4-In AND
 - 4-In NAND
 - 4-In NOR

| Model | Description |
|-------|-------------|
|-------|-------------|

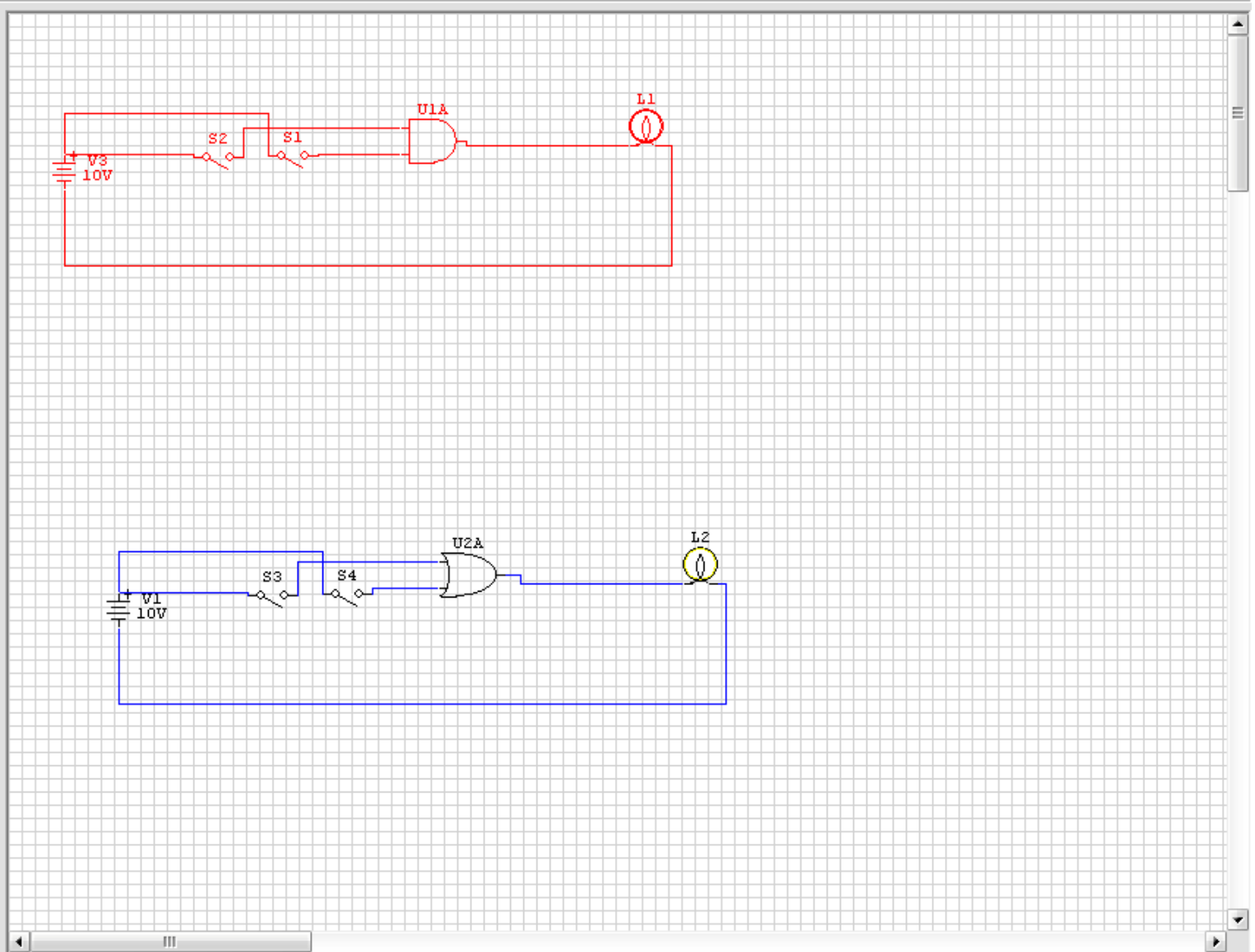

2In OR

